

MINI PROJECT

Write test cases for verifying the fifo who code is mentioned below.

You need to create write task and read task inside the test bench and verify the design. Show the results after running the same in Modelsim/questa Simulation tool.

```
//fifo memory
```

```
module fifo(clk,  
            rst_n,  
            wr,rd,  
            data_in,  
            data_out,  
            fifo_full,  
            fifo_empty);
```

```
parameter FIFO_WIDTH=8;  
parameter FIFO_DEPTH = 16;
```

```
input clk,rst_n,wr,rd;  
input [FIFO_WIDTH-1:0]data_in;  
output fifo_full,fifo_empty;  
output [FIFO_WIDTH-1:0] data_out ;
```

```
reg [FIFO_WIDTH-1:0] data_out;
```

```
reg [FIFO_WIDTH-1:0]mem[FIFO_DEPTH-1:0]; // Memory Dec
```

```
reg [3:0]wr_ptr,rd_ptr,wr_rd_ptr_diff;
```

```
integer i;
```

```
reg [3:0]count,count1;
```

```
wire fifo_full = (wr_ptr == 4'd0 & wr_rd_ptr_diff == 4'd14) ? 1 : 0;
```

```
wire fifo_empty = (rd_ptr== 4'd0 & wr_rd_ptr_diff == 4'd0) ? 1 : 0;
```

```
always @ (posedge clk or negedge rst_n)
```

```
begin
```

```
if(!rst_n)
```

```
begin
```

```
for(i=0;i<=15;i=i+1)
```

```
mem[i]<=8'd0;
```

```
end
```

```
//WRITE PORTION
```

```
else if(wr)
```

```
mem[wr_ptr]<=data_in;
```

```
end
```

```
//Write Ptr
```

```
always @ (posedge clk or negedge rst_n)
```

```
begin
  if(!rst_n)
    wr_ptr <= 4'd0;
  else if(wr)
    wr_ptr <= wr_ptr + 4'd1;
end
```

//READ OPERATION

```
always @ (posedge clk or negedge rst_n)
begin
  if(!rst_n)
    data_out <= 8'd0;
  else if(rd)
    data_out <= mem[rd_ptr];
end
```

//Read Ptr

```
always @ (posedge clk or negedge rst_n)
begin
  if(!rst_n)
    rd_ptr <= 4'd0;
  else if(rd)
    rd_ptr <= rd_ptr + 4'd1;
end
```

//FIFO EMPTY and FULL Logic

```
always @ (posedge clk or negedge rst_n)
begin
```

```
if(!rst_n)
    wr_rd_ptr_diff <= 4'd0;
else if(wr & wr_rd_ptr_diff !=4'd15)
    wr_rd_ptr_diff <= wr_rd_ptr_diff + 4'd1;
else if(rd & wr_rd_ptr_diff != 4'd0)
    wr_rd_ptr_diff <= wr_rd_ptr_diff - 4'd1;
end
```

```
endmodule
```